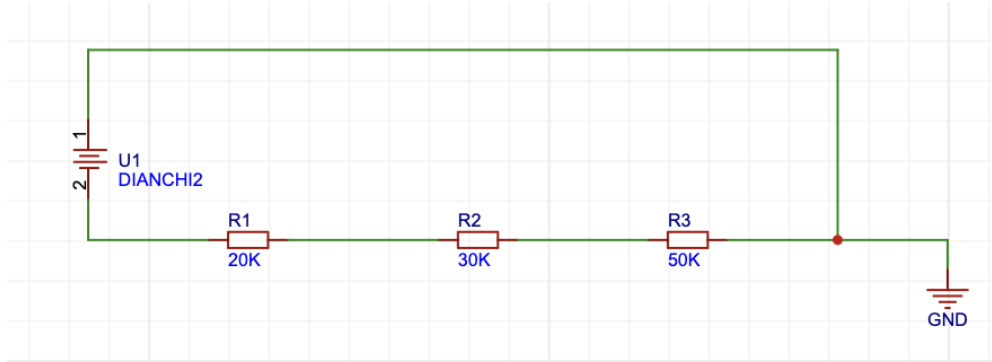


Embedded Systems & IoT April -July 2026

Lab Exercise: Schematics with ESP32


PART B

Circuit connected in series



Ref	Value	Type
U1	DIANCHI2 (battery)	Voltage source
R1	20 k Ω	Resistor
R2	30 k Ω	Resistor
R3	50 k Ω	Resistor
GND	-	Ground symbol

Circuit connected in parallel

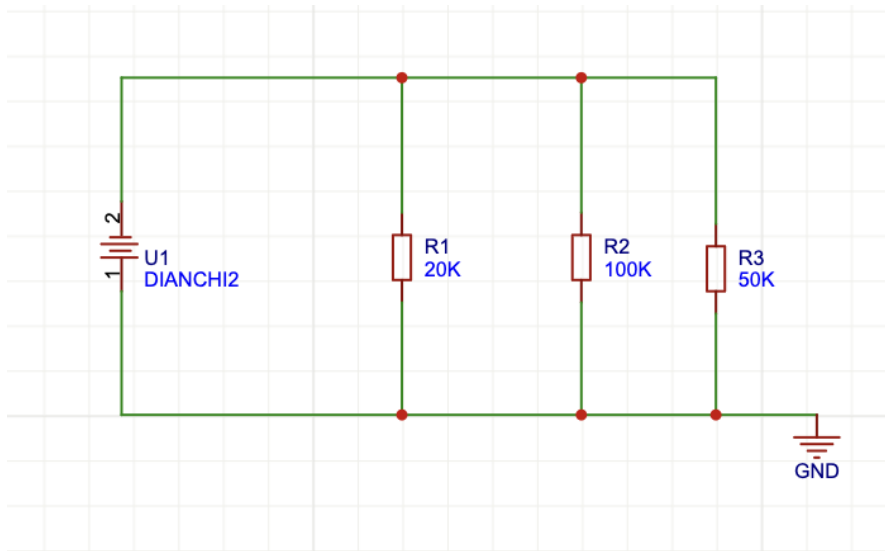

Ref	Value	Type
U1	DIANCHI2 (battery)	Voltage source
R1	20 k Ω	Resistor
R2	100 k Ω	Resistor
R3	50 k Ω	Resistor
GND	-	Ground symbol

